



System-On-Chip Technologies

Contents

1	General	2
2	SoC Paradigm	2
2.1	Moore's Law	2
2.2	Challenges	2
2.3	Chip Platforms	2
2.4	CMOS	2
2.5	MOSFET	3
2.6	Inverter	3
3	SoC Components	3
3.1	Sequential Logic	3
3.2	Karnaugh-Maps	4
3.3	Finite State Machines	4
3.4	Adder	4
3.5	Multipplier (Addition of partial products)	5
3.6	Shifter	5
3.7	Multiplexer	5
4	Processor Structure	5
4.1	Processor Classification	5
4.2	Software Levels	5
4.3	Multi Cycle Core	5
4.4	Hazards (problems due to pipelining)	6
4.5	Processor Performance	6
5	Memory	6
5.1	CMOS Memory	7
5.2	Cache	7
5.3	Branch Prediction	7
5.4	Main Memory	8
5.5	Memory Block	8
5.6	Memory cell types	8
6	Interconnect	9
6.1	Interconnection	9
6.2	AMBA AHB	9
6.3	FIFOs	9
6.4	Network-on-Chips (NoC)	9
7	Low Power Design	9
7.1	Motivation – Why?	9
7.2	Techniques and Hierarchy	9

1. General

10^{\pm}	21	18	15	12	9	6	3	2	1
+	Z zetta	E exa	P peta	T tera	G giga	M mega	k kilo	h hecto	da deca
-	z zepto	a atto	f femto	p pico	n nano	μ micro	m milli	c centi	d deci

2. SoC Paradigm

2.1. Moore's Law

Chip capacity (transistors, performance) doubles every 18–24 month

2.2. Challenges


Optimization: Time-To-Market, Price, Performance, Power Cons.

Productivity: reuse components, shorter development cycles, higher chances for (first time) fault-free design

2.3. Chip Platforms

Computation Density (CD) vs Functional Diversity (FD)

Platform	CD	FC		
CPU	40 – 80	256 – 16k	ALU	
DSP			Multiplier	very f
ASIP			special exec units	few
FPGA	400	1	LUTs	thousa
ASIC	4'000	10	standard cells	million
Custom IC	> 10'000	≈ 0	transistors	10 mil

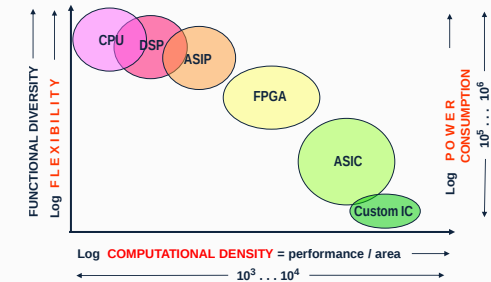

$$CD = \frac{IPC \cdot f \cdot w \cdot \lambda^2}{A}$$


Instructions per cycle IPC, structure size λ , area A

Frequency f , Wordsize w (e.g 32 Bit)

 2.4. CMOS

Complementary Metal (Poly-Si) Oxide (SiO₂) Semiconductor


Why? Low power dissipation, Noise immunity, Clean logic levels, One supply voltage, Cascadable, Easy to design, Fabrication well understood



2.5. MOSFET

channel width	$W_{n/p}$
channel length	$L_{n/p}$
gate oxide thickness	t_{ox}
electron mobility	$\mu_n \approx 250 \times 10^{-4} \frac{m^2}{Vs}$ $\mu_p \approx 200 \times 10^{-4} \frac{m^2}{Vs}$
rel. permittivity of gate oxide	$\epsilon_{ox} \approx 3,9$
dielectric constant	$\epsilon_0 = 8.854 187 8 \times 10^{-12} \frac{As}{Vm}$
specific oxide capacity	$C'_{ox} = \frac{\epsilon_{ox}\epsilon_0}{t_{ox}}$
oxide capacity	$C_{ox} = C'_{ox} \cdot WL$
gain (also β)	$K_n = \mu_n C'_{ox} \frac{W_n}{L_n}$ $K_p = (-1)\mu_p C'_{ox} \frac{W_p}{L_p}$
propagation delay	$t_{pHL} \propto \frac{C_L t_{ox} L_p}{W_p \mu_p \epsilon_{ox} (V_{DD} - V_{th})}$

2.6. Inverter

 

Dynamic Power Consumption

$$P_{dyn} = P_{cap} + P_{short}$$

Capacity Power


$$P_{cap} = \alpha_{01} f C_L V_{DD}^2$$

Short Circuit Power:

$$P_{short} = \alpha_{01} f \beta_n \tau (V_{DD} - 2V_{th})^3$$

3. SoC Components

3.1. Sequential Logic

 

Flip-flop characteristics:

- setup-time: Data must be stable t_{setup} before clock edge
- hold-time: Data must be stable for t_{hold} after clock edge
- clock-to-output delay: Data will be visible at output t_{c2q} after clock edge

t_{Setup}	setup before clock edge
t_{hold}	hold after clock edge
t_{c2q}	output valid after t_{c2q}
Max. clock period	$t_{clk} \geq t_{1,c2q} + t_{logic,max} + t_{2,setup}$
Max. clockfrequency	$f_{max} = \left\lfloor \frac{1}{t_{clk}} \right\rfloor$ (Nicht aufrunden)
hold time condition	$t_{hold} \leq t_{c2q} + t_{logic,min} \rightarrow$ Dummy Gate
Durchsatz	$\frac{1 \text{ Sample}}{t_{clk,pipe}} = f$
Latenz	$t_{clk} \cdot \# \text{Pipelinstages} (\#FFs - 1)$
Slack	$t_{slack} = t_{available} - t_{required}$


3.2. Karnaugh-Maps

$z \backslash xy$	00	01	11	10
0	1	0	0	0
1	X	1	1	0




Combine equal cells:
 e.g. $\overline{xy} + y \cdot z$
 Use don't care values!

3.3. Finite State Machines

Moore Automat

 

Mealy Automat

   


Synchronous System Design paradigm: Essentially all control functions in state-of-art digital IC's consist of "communicating FSMs".

Avoid combinatorial logic through paths!

Stick to one FSM design style across SoC!

3.4. Adder

 

3.4.1 Ripple-Carry

Worst-Case ($G, P = 1$): $t_{add} = (N - 1)t_{carry} + t_{sum}$
 Number of input Bits/Full Adders N

3.4.2 Carry-Bypass

Fast carry propagation (useful if $N > 4$)

$t_{CBA} = t_{setup} + Bt_{carry} + (\frac{N}{B} - 1)t_{skip} + (B - 1)t_{carry} + t_{sum}$
 with group size in bits B . t_{CBA} still $\mathcal{O}(N)$, but with more graduate slope

3.4.3 Carry-Select

Precompute C_{out} for $C_{in} = 0$ and $C_{in} = 1$ for all blocks in parallel. Then select the correct one. $t_{CSA} = t_{setup} + Bt_{carry} + \frac{N}{B}t_{mux} + t_{sum}$
 Square Root Carry-Select Adder:


$$t_{SCS} = t_{setup} + Mt_{carry} + \sqrt{2N}t_{mux} + t_{sum}$$

3.5. Multiplier (Addition of partial products)

$$x \cdot y = \sum_{j=0}^{M-1} \sum_{i=0}^{N-1} x_i y_j \cdot 2^{i+j} \quad \text{Result requires } N + M \text{ bit}$$

3.5.1 Repeated Addition

3.5.2 Sequential: Right Shift and Add

 

3.5.3 Array Multiplier

All partial products generated in parallel and organized in adder array with respective offset

$$t_{mul} = [(M - 1)(N - 2)]t_{carry} + (N - 1)t_{sum} + t_{and}$$

3.6. Shifter

Single-bit left/ right shift operations through individual pass transistors
Barrel Shifter: Words pass through maximum one transmission gate

3.7. Multiplexer


$$\text{Mux: } Z = \bar{S}A_1 + SA_1 \quad \text{DeMux: } Z_1 = \bar{S}A, \quad Z_2 = SA$$

4. Processor Structure

4.1. Processor Classification

	Type	Application	Characteristic	Remark
Instruction complexity	RISC	Embedded control	Load/store instructions for memory access	MIPS, ARM, PowerPC
	CISC	Personal Computer/ Servers	Complex, variable-length instructions	Intel x86-based
Instruction-level parallelism (ILP)	Superscalar	Personal Computer/ Embedded	Instruction parallelism on run-time	Intel, ARM, PowerPC
	VLIW	Image Processing	Instruction parallelism on compile-time	Parallel video pixel processing
Application-specific area	ASIP	Embedded	Application-specific instructions	Tensilica
	DSP	Signal Processing	HW multiply for digital filters	TI

4.2. Software Levels

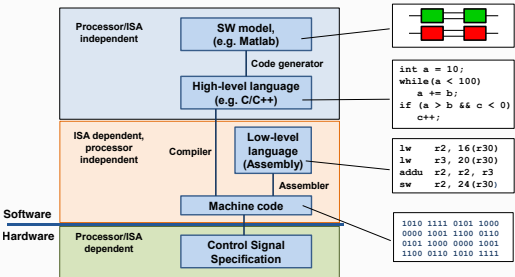


4.3. Multi Cycle Core

1. **Instruction Fetch (IF):** increase PC
2. **Instruction Decode (ID):** read OP and register
3. **Execution (EX):** ALU executes command
4. **Memory Stage (M):** read/write to memory
5. **Write Back (WB):** load from memory to register?

 
4.4. Hazards (problems due to pipelining)

Structural Hazard: same resource is needed multiple times in the same cycle




Data Hazard: data dependencies (read-after write, write-after-write, write-after-read).

 Solution: Forwarding, Stalling, Scheduling




Stalling is required

 

With register forwarding: Only 1 stall below EX.

Control Hazard: next executed instruction is not the next specified instruction due to jump, branch, exception.


Solution: Branch predictor

 

4.5. Processor Performance

$$\text{CPU Time} = \underbrace{\frac{\text{Instructions}}{\text{Program}}}_{\text{Estimate}} \cdot \underbrace{\frac{\text{Clock Cycles}}{\text{Instruction}}}_{\text{CPI}} \cdot \underbrace{\frac{\text{Seconds}}{\text{Clock Cycle}}}_{\frac{1}{f_{\text{CPU}}}}$$

5. Memory

 

Type	Used	Speed	Density
Register	CPU Registers 32 · 64 bit	< ns	
On-Chip SRAM	Cache 32 kByte	ns	
DDR3 SDRAM	Main Memory ≈ GByte	2 · 800 MHz	
HDD	Mass Storage > TB	150 $\frac{\text{MB}}{\text{s}}$	
ROM	Sys. Config few kByte	≈ kB/s	

5.1. CMOS Memory


Register: 2 Inverters (Q, \bar{Q})

Latch: 4 NANDS (e, D, Q, \bar{Q})

Flip-Flop: (Q, \bar{Q}, clk)

 5.2. Cache

Caches store only small share of main memory. The Cache maps RAM-Addresses to Cache-Entries. One Cache-Entry can contain several Data Bytes. The Tag verifies the mapping, the Valid-Flag verifies the actuality of the cached data.



$$\#RAMAddressBits = \#TagBits + \#IndexBits + \#OffsetBits$$

$$\#CacheEntries = 2^{\#Indexbits}$$

$$\#CacheDataBytes = 2^{\#Offsetbits} \quad (\text{Byte accurate Cache access})$$



$$CacheSizeInByte = \#CacheEntries \cdot \#CacheDataBytes$$

5.2.1 Direct Mapped Cache

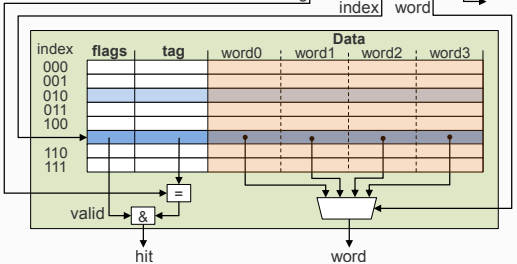 Example: 16 KB direct mapped

4 words à 32 bit per cache line

- 10 bit index (1k cache lines)
- 18 bit tag
- 4 bit offset (for word and byte)



Replace Strategy: Replace old with new.

5.2.2 Set-Associative-Cache

Blocks with equal Index can be stored in n cache entries. Tag needed to distinguish. Replace Strategy: Replace if all sets are full. Random, FIFO or LRU (least recently used)

$$\frac{\#Zugriffe}{Zeit} = \text{Hit-Rate} \cdot \text{Hit-Time} + \text{Miss-Rate} \cdot \text{Miss-Time}$$

5.2.3 Fully Associative Cache

A memory block can be stored in any cache entry.

5.3. Branch Prediction

• 2-bit prediction


```
0x400258: lw    r2, 24(r30)
0x400260: sli   r3, r2, 15
0x400268: bne   r3, r0, 400280
```




• 1-bit prediction

- 1 – taken
- 0 – not taken

Branch history table

 


5.4. Main Memory

 

$$\Delta V = (V_X - V_{Pre}) \cdot \frac{C_S}{C_S + C_{BL}} \quad V_{Pre} \approx 0.5 V_{DD}$$


$$\Delta V_{BL} = V_{eq} - V_{BL} = \pm \frac{C_S}{C_S + C_{BL}} \cdot \frac{V_{DD}}{2}$$

5.5. Memory Block

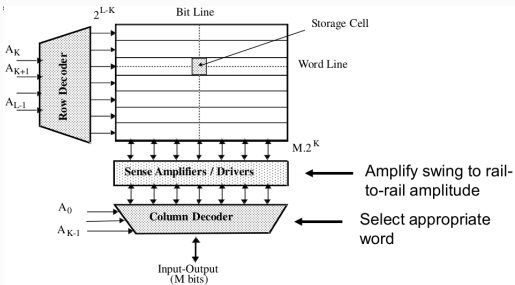


5.6. Memory cell types


DRAM

 


SRAM

 

Flash

 

ROM

 

DRAM Timings: $t_{CAS} - t_{RCD} - t_{RP} - t_{RAS}$

Access Latency: $t_{Lat} = t_{CAS} + t_{RCD}$

Min. row cycle: $t_{RC} = t_{RP} + t_{RAS}$

Access Times:


DRAM:	Single:	$(cLatency + 1c(amp)) \cdot \#reads$
	Burst:	$cLatency + (\#reads-1) + 1c(amp)$
SRAM	Single:	$cLatency \cdot \#reads$
	Burst:	$cLatency + (\#reads-1)$

6. Interconnect

6.1. Interconnection

 6.1.1 Processor Local Bus (PLB)

Bus-Transaction: Request → Addr. Trans. → Data Trans. → Data Ack
Burst Transfer: Reduction of Req./Addr. signaling overhead for read/write transactions to consecutive addresses. Burst transfers with implicit address increment



Bus Standard: AMBA (ARM), CoreConnect (IBM), OCP (Sonics), VSIA

6.2. AMBA AHB

Advanced Microcontroller Bus Architecture Advanced eXtensible Interface

6.3. FIFOs

Are used for decoupling clock domains or word widths.

Pointer: Read (RP) and Write (WP)

Control Flags: Almost Full (AF) and almost empty (AE)

6.4. Network-on-Chips (NoC)

Benefits: Scalability, Synchronization, short point-to-point links

Drawbacks: Latency, Area

7. Low Power Design

7.1. Motivation – Why?

- Reliability: Plus 10C doubles failure rate
- High currents destroy on-chip wires
- Cooling: higher costs and power consumption

Leakage current: $I_{leak} \propto \exp(V_{GS} - V_{th})$

Gate Delay: $t_d \propto \frac{C_L}{V_{DD} - V_{th}}$

7.2. Techniques and Hierarchy

Trade in Power with Performance, Area, Cost

Frequency Scaling and Voltage Scaling (DFS, DVS)

Algorithmic Optimization: $x^2 + ax = x(x + a)$

Power Gating: Switch components off if not needed.

Clock Gating: toggle registers only when outputs can change

Threshold Control: bias threshold voltage V_{th}